

Physics ~~Part~~  
 Test Question &  
 Answer

Q1 (a) using relevant equations, define the following terms

- (i) current
- (ii) Resistance
- (iii) Electromotive force

Soln.

(i) current is the rate of flow of electric charge on the quantity of electrons passing a given point, which can be mathematically express as;

$$I = \frac{Q}{t} \text{ (A)}$$

(ii) Resistance is the opposition flow of charge measured in Ohm's ( $\Omega$ ), which can be mathematically express as;

$$R = \frac{PL}{A} \text{ (}\Omega\text{)}$$

(iii) Electromotive force: It is the potential difference of a cell when its not connected to any external circuit, which can be mathematically express as;

$$\Sigma = IR + Ir$$

(Q1b) An electricity supply cable consists of a steel core of cross sectional area of  $50\text{mm}^2$  with six other aluminum conductors of the same cross sectional area arranged around it; cal. the resistance of a

120 m length of the cable (1)  
 (Take density of steel =  $9.0 \times 10^6$  and density of Al =  $2.5 \times 10^8$  gm  
 soln

Resistance of steel cable  $R_s$ ,

$$R_s = \frac{PL}{A} = \frac{9 \times 10^6 \times 120}{50 \times 10^{-6}} = 21.6$$

Resistance of 6 aluminium cable


$$R_A = \frac{PL}{A} = \frac{2.5 \times 10^8 \times 120}{6 \times 50 \times 10^{-6}} = 0.01$$

effective resistance of the cable  $R_c$ ;

$$\frac{1}{R_c} = \frac{1}{R_s} + \frac{1}{R_A}$$

$$\frac{1}{R_c} = \frac{1}{21.6} + \frac{1}{0.01} = 100 \Omega$$

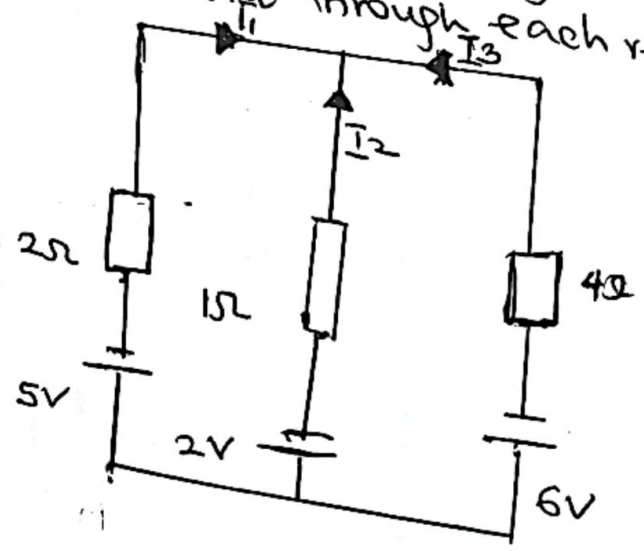Q2. Using nodal analysis, cal. the current through each resistor



$I_1$   $I_2$

Soln.

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3}$$

$$\frac{(-5 - V_A)}{R_1} + \frac{(-2 - V_A)}{R_2} + \frac{(-6 - V_A)}{R_3}$$

$$\frac{(-5 - V_A)}{2} + \frac{(-2 - V_A)}{1} + \frac{(-6 - V_A)}{4}$$

$$2(-5 - V_A) + 4(-2 - V_A) + (-6 - V_A) = 0$$

$$-10 - 2V_A - 8 - 4V_A - 6 - V_A = 0$$

$$-24 - 7V_A = 0$$

$$\frac{-24}{7} = \frac{7V_A}{7} \quad V_A = -3.4V$$

$$I_1 = \frac{-5 - (-3.4)}{2} = -0.8A$$

$$I_2 = \frac{-2 - (-3.4)}{1} = 1.4A$$

$$I_3 = \frac{-6 - (-3.4)}{4} = -0.6A$$

Proof.  $I_1 + I_2 + I_3 = 0$

$$-0.8 + 1.4 + (-0.6) = 0$$

(2bi) Show that for a pure inductive circuit, the voltage leads the current by  $\pi/2$ .  
 Int: An value of

Soln.

$$I = I_0 \sin 2\pi ft$$

$$V = V_0 \sin (2\pi ft + \pi/2)$$

voltage lead by  $\pi/2$

(2bi) obtain the corresponding expression for inductive reactance  $X_L$  and rms current  $I_{rms}$ .

Soln.

$$X_L = 2\pi fL \text{ - Inductive reactance}$$

$$I_{rms} = I = \frac{I_0}{\sqrt{2}}$$

3a. A coil has an inductance of 0.3 H. Determine the values of the peak voltage and current in the circuit of 240 V and 50 Hz.  
 Soln.

$$\text{Peak voltage} = V = \frac{V_0}{\sqrt{2}}$$

$$= 240 = \frac{V_0}{\sqrt{2}}$$

$$V_0 = 240 \times \sqrt{2}$$

$$V_0 = 339.4V$$

$$\text{Peak current} = I = \frac{I_0}{\sqrt{2}}$$

② 7. An ac voltage whose peak value is 80 volts is connected across 60Ω resistor. The values of  $I_{rms}$  and  $V_{rms}$  are?

Soln.

$$V_0 = I_0 R = \frac{V_0}{R} = \frac{I_0 R}{R}$$

$$I_0 = \frac{V_0}{R} = \frac{80}{60} = 1.33A$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} = \frac{1.33}{\sqrt{2}}$$

$$I_{rms} \times \sqrt{2} = I_0 = 1.33$$


$$1.33 \times \sqrt{2} = 1.88 = 0.94$$

$$V_{rms} = \frac{80}{\sqrt{2}} = 56.56$$

8. In a pure capacitive circuit, the current lags the voltage by  $90^\circ$ .

9. For a series RLC circuit, the expression for Impedance  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

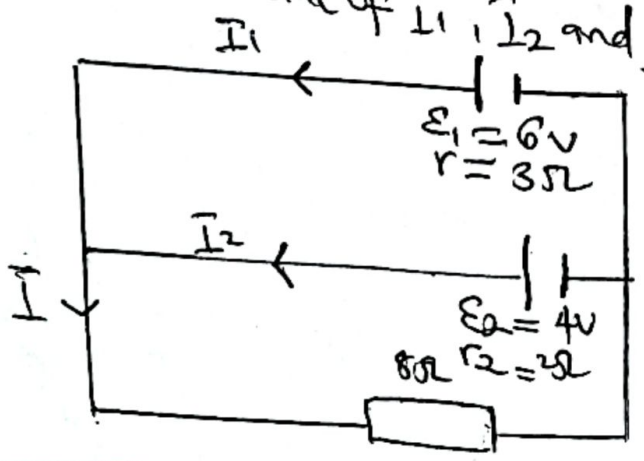10. Use the below figure and determine the value of  $I_1$ ,  $I_2$  and  $I$



Soln.

(4)

$$I = I_1 + I_2 \quad \text{--- (1)}$$

$$E_1 = IR + I_1 r$$

$$6 = (I_1 + I_2) \cdot 8 + I_1 \cdot 3$$

$$6 = 8I_1 + 8I_2 + 3I_1$$

$$6 = 11I_1 + 8I_2 \quad \text{--- (2)}$$

$$E_2 = IR + I_2 R_2$$

$$4 = (I_1 + I_2) \cdot 8 + I_2 \cdot 2$$

$$4 = 8I_1 + 8I_2 + 2I_2$$

$$4 = 8I_1 + 10I_2 \quad \text{--- (3)}$$

$$8 = 11I_1 + 8I_2 \times 8$$

$$4 = 8I_1 + 10I_2 \times 11$$

$$48 = 88I_1 + 64I_2$$

$$44 = 88I_1 + 110I_2$$

$$4 = 0 - 46I_2$$

$$4 = -46I_2$$

$$\frac{4}{-46} = \frac{-46I_2}{-46}$$

$$I_2 = \frac{4}{-46} = -0.087A$$

Sub the value in eqn (2)

$$6 = 11I_1 + 8(-0.087)$$

$$6 = 11I_1 - 0.696$$

$$6 + 0.696 = 11I_1$$

$$6.696 = 11I_1 \quad I_1 = \frac{6.696}{11} = 0.6087A$$

$$V = IR$$

$$I = \frac{V}{R}$$

where  $R = X_L = 2\pi fL$   
 $= 2\pi(50)(0.3)$   
 $R = 94.26$

$$I = \frac{240}{94.26} = 2.55A$$

$$I = \frac{I_0}{\sqrt{2}} = 2.55 = \frac{I_0}{\sqrt{2}}$$

$$I_0 = 2.55 \times \sqrt{2}$$

$$= 3.6A$$

3b. list the four (4) types of transformers and state their respective applications.  
 soln.

- i) step-up transformers
  - ii) step-down transformers
  - iii) Isolation transformers
  - iv) Air core "
- Applications

- $\Rightarrow$  step-up transformers: power distribution
- $\Rightarrow$  step-down transformers: power transmission
- $\Rightarrow$  Isolation transformers: safety purpose insulation barrier
- $\Rightarrow$  Air core transformer: Radio frequency application.

4. The relationship between the length of the conductor, the cross-sectional area and the resistance of the material is given as;  $\rho = \frac{RA}{L}$

5. A 12k $\Omega$  and 8k $\Omega$  resistors are connected in series to a 99V battery. The p.d across the 12k resistor is?

soln.

$$V = IR \quad R_T = R_1 + R_2 \quad R_T = 20k\Omega$$

$$99 = I \cdot 20$$

$$R_T = R_1 + R_2 + \dots + R_n$$

$$R_T = 12 + 8$$

$$R_T = 20k\Omega$$

$$V = IR$$

$$99 = I \cdot 20$$

$$I = \frac{99}{20} = 4.95A$$

The p.d across 12k $\Omega$

$$V = IR$$

$$V = 4.95 \times 12$$

$$V = 59.4V$$

6. Kirchhoff's second law states that; The algebraic sum of the emf is equal to the algebraic sum of the product of the current and resistance.

$$\sum \mathcal{E} = \sum (IR)$$

$$\bar{I} = ?$$

$$V = \bar{I} R$$

$$\bar{I} = \frac{V}{R}$$

$$\text{where } R = X_L = 2\pi fL \\ = 2\pi(50)(0.3) \\ R = 94.26$$

$$\bar{I} = \frac{240}{94.26} = 2.55A$$

$$\bar{I} = \frac{\bar{I}_0}{\sqrt{2}} = 2.55 = \frac{\bar{I}_0}{\sqrt{2}}$$

$$\bar{I}_0 = 2.55 \times \sqrt{2} \\ = 3.6A$$

3b. list the four (4) types of transformers and state their respective applications.

Soln.

- i) step-up transformers
- ii) step-down transformers
- iii) Isolation transformers
- iv) Air core "

Applications

⇒ step-up transformers: power distribution

⇒ step-down transformers: power transmission

⇒ Isolation transformers: safety purpose insulation barrier

⇒ Air core transformer: Radio frequency application.

4. The relationship between length,  $l$  cross sectional area,  $A$  and the resistance of the material is given as;  $R = \frac{\rho l}{A}$

5. A  $12k\Omega$  and  $8k\Omega$  resistors are connected in series to a  $90V$  battery. The p.d across the  $12k\Omega$  resistor is?

Soln.

$$V = \bar{I} R \quad R_T = R_1 + R_2 + \dots + R_n \\ 90 = \bar{I} \cdot 20$$

$$R_T = R_1 + R_2 + \dots + R_n$$

$$R_T = 12 + 8$$

$$R_T = 20k\Omega$$

$$V = \bar{I} R$$

$$90 = \bar{I} 20$$

$$\frac{90}{20} = \frac{\bar{I} 20}{20} \quad \bar{I} = \frac{90}{20} = 0.45A$$

The p.d across  $12k\Omega$

$$V = \bar{I} R$$

$$V = 0.45 \times 12$$

$$V = 5.4V$$

6. Kirchhoff's second law states that; The algebraic sum of the emf is equal to the algebraic sum of the product of the current and resistance.

$$\sum \varepsilon = \sum (IR)$$

$$I = I_1 + I_2$$

$$\bar{I} = 0.609 + (-0.087)$$

$$\bar{I} = 0.609 - 0.087$$

$$\bar{I} = 0.522$$

$$\therefore \bar{I} = 0.522 \text{ A}$$

$$\bar{I}_1 = 0.609 \text{ A}$$

$$\bar{I}_2 = -0.087 \text{ A}$$

11. A  $100 \mu\text{F}$  capacitor is connected to a  $12\text{V}$  battery, a frequency of  $50\text{Hz}$ . The values of  $X_c$  and  $I_c$  are?

Soln.

$$X_c = \frac{1}{2\pi fC}$$

$$X_c = \frac{1}{2 \times 3.142 \times 50 \times 100 \times 10^{-6}}$$

$$X_c = \underline{\underline{31.82 \Omega}}$$

$$I_c = \frac{V}{X_c} = \frac{12}{31.82} = \underline{\underline{0.377 \text{ A}}}$$